

VC State Variable Filter and 1v/oct quadrature vco

2003-03-12 Jonatan Liljedahl <than@techno.org>
 TL074 and SSM2164 Power: +/- 15V

1v/oct calibration:
 Input 1V on CV2
 adjust cutoff-pot for 0.000V at TP
 change the input on CV2 from 1V to 0V
 adjust trimpot for 0.187V at TP

